 



# Digital Electronics

## Shift Registers


 
## Basic Shift Register Operations


A shift register is an arrangement of flip-flops with important applications in storage and movement of data. Some basic data movements are illustrated here.


 
## Serial-in/Serial out Shift Register

Shift registers are available in IC form or can be constructed from discrete flip-flops as is shown here with a five-bit serial-in serial-out register.

Each clock pulse will move an input bit to the next flip-flop. For example, a 1 is shown as it moves across.




## A Basic Application

An application of shift registers is conversion of serial data to parallel form.


For example, assume the binary number 1011 is loaded sequentially, one bit at each clock pulse.

 After 4 clock pulses, the data is available at the parallel output.


 
## The 74HC164A Shift Register

The 74HC164A is a CMOS 8-bit serial in/parallel out shift register.  $V_{CC}$  can be from +2.0 V to +6.0 V.




One of the two serial data inputs may be used as an active HIGH enable to gate the other input. If no enable is needed, the other serial input can be connected to  $V_{CC}$ . The 74HC164A has an active LOW asynchronous clear. Data is entered on the leading-edge of the clock.
 
## Waveforms for the 74HC164A


Sample waveforms for the 74HC164A are shown. Notice that  $B$  acts as an active HIGH enable for the data on  $A$  as discussed.

As with CMOS devices, unused inputs should *always* be connected to a logic level; unused outputs should be left open.



 
## Parallel in/Serial out Shift Register

Shift registers can be used to convert parallel data to serial form. A logic diagram for this type of register is shown:


 
## The 74HC165 Shift Register


The 74HC165 is a CMOS 8-bit parallel in/serial out shift register. The logic symbol is shown:



The clock ( $CLK$ ) and clock inhibit ( $CLK\ INH$ ) lines are connected to a common OR gate, so either of these inputs can be used as an active-LOW clock enable with the other as the clock input. Data is loaded *asynchronously* when  $SH/\overline{LD}$  is LOW and moved through the register *synchronously* when  $SH/\overline{LD}$  is HIGH and a rising clock pulse occurs.

 
# The 74HC165 Shift Register

A Multisim simulation of the 74165A is shown. The word generator is used as a source for the pattern shown in the green probes.


 
## The 74HC165 Shift Register


Here the scope is opened and you can observe the pattern. The MSB is HIGH and is on the  $Q_7$  output as soon as LOAD is LOW.


 
## Bidirectional Shift Register

Bidirectional shift registers can shift the data in either direction using a *RIGHT/LEFT* input.


The logic analyzer simulation shows a bidirectional shift register such as the one shown in Figure 9-19 of the text. Notice the HIGH level from the Serial data in is shifted at first from  $Q_3$  toward  $Q_0$ .



## Bidirectional Shift Register


**Question** How will the pattern change if the *RIGHT/LEFT* control signal is inverted?

**Answer** See display

 

 
## Universal Shift Register

A universal shift register has both serial and parallel input and output capability. The 74HC194 is an example of a 4-bit bidirectional universal shift register.



Sample waveforms are on the following slide...


# Universal Shift Register

 

 
## Shift Register Counters

Shift registers can form useful counters by recirculating a pattern of 0's and 1's. Two important shift register counters are the *Johnson counter* and the *ring counter*.

The Johnson counter can be made with a series of D flip-flops




 ... or with a series of J-K flip flops. Here  $Q_3$  and  $\bar{Q}_3$  are fed back to the  $J$  and  $K$  inputs with a “twist”.


 
## Johnson Counter

Redrawing the same Johnson counter (without the clock shown) illustrates why it is sometimes called as a “twisted-ring” counter.



## Johnson Counter

The Johnson counter is useful when you need a sequence that changes by only one bit at a time but it has a limited number of states ( $2n$ , where  $n$  = number of stages).

The first five counts for a 4-bit Johnson counter that is initially cleared are:

CLK	$Q0$	$Q1$	$Q2$	$Q3$
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1


## Question

What are the remaining 3 states?

 
## Ring Counter

The ring counter can also be implemented with either D flip-flops or J-K flip-flops.

Here is a 4-bit ring counter constructed from a series of D flip-flops. Notice the feedback.



 Like the Johnson counter, it can also be implemented with J-K flip flops.




## Ring Counter

Redrawing the Ring counter (without the clock shown) shows why it is a “ring”.


The disadvantage to this counter is that it must be preloaded with the desired pattern (usually a single 0 or 1) and it has even fewer states than a Johnson counter ( $n$ , where  $n = \text{number of flip-flops}$ ).

 On the other hand, it has the advantage of being self-decoding with a unique output for each state.


 
## Ring Counter

A common pattern for a ring counter is to load it with a single 1 or a single 0. The waveforms shown here are for an 8-bit ring counter with a single 1.



## Shift Register Applications



Shift registers can be used to delay a digital signal by a predetermined amount.

**Example** An 8-bit serial in/serial out shift register has a 40 MHz clock. What is the total delay through the register?
  
## Solution

The delay for each clock is  $1/40 \text{ MHz} = 25 \text{ ns}$


The total delay is  
 $8 \times 25 \text{ ns} = 200 \text{ ns}$


 
## Shift Register Applications

A UART (Universal Asynchronous Receiver Transmitter) is a serial-to-parallel converter and a parallel to serial converter.


UARTs are commonly used in small systems where one device must communicate with another. Parallel data is converted to asynchronous serial form and transmitted. The serial data format is:


 
## Keyboard Encoder

The keyboard encoder is an example of where a ring counter is used in a small system to encode a key press.

Two 74HC195 shift registers are connected as an 8-bit ring counter preloaded with a single 0. As the 0 circulate in the ring counter, it “scans” the keyboard looking for any row that has a key closure. When one is found, a corresponding column line is connected to that row line. The combination of the unique column and row lines identifies the key. The schematic is shown on the following slide...



# Key Terms

**Register** One or more flip-flops used to store and shift data.




**Stage** One storage element in a register.

**Shift** To move binary data from stage to stage within a shift register or other storage device or to move binary data into or out of the device.

**Load** To enter data in a shift register.


**Bidirectional** Having two directions. In a bidirectional shift register, the stored data can be shifted right or left.

   1. The shift register that would be used to delay serial data by 4 clock periods is



 
2. The circuit shown is a

- serial-in/serial-out shift register
- serial-in/parallel-out shift register
- parallel-in/serial-out shift register
- parallel-in/parallel-out shift register



3. If the *SHIFT/LOAD* line is HIGH, data

 - a. is loaded from  $D_0, D_1, D_2$  and  $D_3$  immediately
- b. is loaded from  $D_0, D_1, D_2$  and  $D_3$  on the next CLK
- c. shifted from left to right on the next CLK
- d. shifted from right to left on the next CLK




4. A 4-bit parallel-in/parallel-out shift register will store data for

- a. 1 clock period
- b. 2 clock periods
- c. 3 clock periods
- d. 4 clock periods

5. The 74HC164 (shown) has two serial inputs. If data is placed on the *A* input, the *B* input

 - a. could serve as an active LOW enable
- b. could serve as an active HIGH enable
- c. should be connected to ground
- d. should be left open



6. An advantage of a ring counter over a Johnson counter is that the ring counter


- a. has more possible states for a given number of flip-flops
- b. is cleared after each cycle
- c. allows only one bit to change at a time
- d. is self-decoding

7. A possible sequence for a 4-bit ring counter is

- a. ... 1111, 1110, 1101 ...
- b. ... 0000, 0001, 0010 ...
- c. ... 0001, 0011, 0111 ...
- d. ... 1000, 0100, 0010 ...


8. The circuit shown is a

 - a. serial-in/parallel-out shift register
- b. serial-in/serial-out shift register
- c. ring counter
- d. Johnson counter



9. Assume serial data is applied to the 8-bit shift register shown. The clock frequency is 20 MHz. The first data bit will show up at the output in

- 50 ns
- 200 ns
- 400 ns
- 800 ns

 

10. For transmission, data from a UART is sent in

- a. asynchronous serial form
- b. synchronous parallel form
- c. can be either of the above
- d. none of the above